

# Correction of the final exam. STRM1. (S1/24/25)

Exercise 1:

1.1  $A = (42)_{10} = (?)_2 = (?)_8$

$A = (42)_{10} = (101010)_2 = (52)_8$

$B = (1101010)_6 = (?)_2 = (?)_8$

$1101010$   
 $G_7 G_6 G_5 G_4 G_3 G_2 G_1$

$B_7 = G_7 = 1$

$B_6 = G_6 \oplus B_7 = 0$

$B_5 = G_5 \oplus B_6 = 0$

$B_4 = G_4 \oplus B_5 = 1$

$B_3 = G_3 \oplus B_4 = 1$

$B_2 = G_2 \oplus B_3 = 0$

$B_1 = G_1 \oplus B_2 = 0$

$B = (1001100)_2 = (?)_8$

$1001100$   
 $114$

$B = (114)_8$

$C = (0001000000011)_{BCD} = (?)_2 = (?)_8$

$C = (?)_{10}$

$C = (103)_{10} = (?)_2$

$C = (1100111)_2 = (147)_8$

$103 \div 2 = 51 \text{ r } 1$   
 $51 \div 2 = 25 \text{ r } 1$   
 $25 \div 2 = 12 \text{ r } 1$   
 $12 \div 2 = 6 \text{ r } 0$   
 $6 \div 2 = 3 \text{ r } 0$   
 $3 \div 2 = 1 \text{ r } 1$   
 $1 \div 2 = 0 \text{ r } 1$

1.2  $S_1 = A + C$

$A = (101010)_2 = (00101010)_2 = (00101010)_2$

$C = (1100111)_2 = (01100111)_2 = (01100111)_2$

$A + C = 00101010 + 01100111 = ?$

$(+) + (+) = (-) \Rightarrow \text{overflow}$

$00101010$   
 $+ 01100111$   
 $10010001$

$$S_2 = -A \oplus B = ?$$

$$-A - B = (-A)_{C_2} + (-B)_{C_2} = ?$$

$$A = 101010 = (00101010)_2 \Rightarrow -A = (\overset{\substack{\uparrow \\ \text{hit} \\ \text{sign}}}{1}0101010)_2 = (?)_{C_2}$$

$$|10101010| = 0101010$$

$$(0101010)'' = 1010101 + 1 = 1010110$$

$$(-A)_{C_2} = (11010110)_{C_2}$$

$$B = 1001100 = (01001100)_2 \Rightarrow -B = (\overset{\substack{\uparrow \\ \text{hit} \\ \text{sign}}}{1}1001100)_2 = (!)_{C_2}$$

$$|11001100| = 1001100$$

$$(1001100)'' = 0110011 + 1 = 0110100$$

$$(-B)_{C_2} = (10110100)_{C_2}$$

$$(-A)_{C_2} + (-B)_{C_2} = ?$$

$$\begin{array}{r} 11010110 \\ + 10110100 \\ \hline 110001010 \end{array}$$

↑  
rejected

$$(-) + (-) = (-)$$

$$\Rightarrow \text{No overflow.}$$

2) ASCII code of the word 'EXAM'.

$$E \ X \ A \ M.$$

$$(45)_{16} (58)_{16} (41)_{16} (4D)_{16}$$

So  
(1)

$$EXAM = 4558414D$$

3)  $N_1 = 41DC0000$

$$N_1 = (?)_{10}$$

01000001110111000000000000000000															
hit sign				exp		M									

$$exp_8 = 10000011 = (131)_{10} \Rightarrow exp_r = 131 - 127 = 4$$

$$N_1 = 1,10111 \times 2^4 = 11011,1 = 1 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0$$

$$= (27,5)_{10}$$

$$N_2 = (!)_{10}$$

$$N_2 = C1480000$$

$$N_2 = (?)_{10}$$

$$N_2 = \boxed{11000001010010000 \dots 0}$$

$$\text{exp}_B = 1000010 = (130)_{10} \Rightarrow \text{exp}_r = 130 - 127 = 3.$$

$$N_2 = -1,1001 \times 2^3 = -1100,1 = -(1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^{-1}) = (12,5)_{10}$$

$$3.2. S = N_1 + N_2 = ?$$

$$S = 1,10111 \times 2^4 - 1,1001 \times 2^3 = (11,0111 - 1,1001) \times 2^3$$

$$\begin{array}{r} 11,0111 \\ - 1,1001 \\ \hline 01,1110 \end{array}$$

$$S = 1,111 \times 2^3 = ? \text{ condensed form in Hexadecimal?}$$

$$\text{exp} = 3 \Rightarrow \text{exp}_B = 127 + 3 = (130)_{10} = (1,0000010)_2$$

$$M = 111$$

$$S = \boxed{0100000101110 \dots 0}$$

$$S = 41.700000$$

### Exercise 2:

1) 1.1 Expression for F.


$$F = (a \oplus b) + (\overline{c \oplus d}) + (a \cdot c \cdot d) + (\bar{a} \cdot c \cdot d) + (a \bar{b} \bar{c}) + (a \cdot c \cdot \bar{b})$$

1.2. Simplification:

$$\begin{aligned} F &= \bar{a}b + a\bar{b} + \bar{c}\bar{d} + cd + acd + \bar{a}cd + a\bar{b}\bar{c} + a\bar{c}\bar{b} \\ &= \bar{a}b + a\bar{b} + \bar{c}\bar{d} + cd + (\bar{a} + a)cd + a\bar{b}(c + \bar{c}) \\ &= \bar{a}b + a\bar{b} + \bar{c}\bar{d} + cd + cd + a\bar{b} \end{aligned}$$

$$F = a \oplus b + \overline{c \oplus d}$$

1.3 circuit

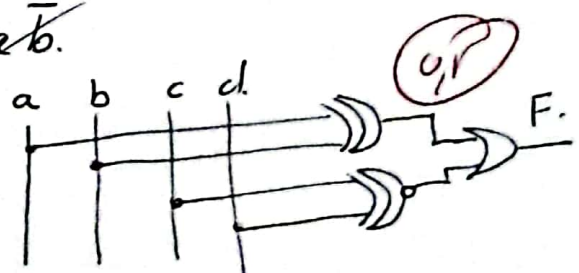



$$2) S = (a+b+c)(\bar{a}+b+c) + ab + bc$$

2.1) Truth Table

a	b	c	s
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2.2)

		b	c
a	0	1	1
	1	0	1

$$S = b + c$$

2.3) S using algebraic methods.

$$\begin{aligned}
 S &= ab + ac + b\bar{a} + c\bar{a} + cb + c + ab + bc \\
 &= c(a + \bar{a}) + b(a + \bar{a}) + c(b + 1) \\
 &= c + b + c = b + c
 \end{aligned}$$

Exercise 3.:

1) Truth Table:

A	B	C	D	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	1	0
1	1	0	0	0	1	1
1	1	0	1	0	1	1
1	1	1	0	0	1	1
1	1	1	1	1	0	0

2) Simplified disjunctive equations of S<sub>2</sub>, S<sub>1</sub> and S<sub>0</sub>.

$$S_2 = ABCD$$

S<sub>1</sub>, S<sub>1</sub> = ?

		CD	00	01	11	10
AB	00				1	
	01		1	1		1
	11	1	1			1
	10		1		1	1

$$\begin{aligned}
 S_1 &= AB\bar{D} + \bar{B}CD + \bar{A}BD + A\bar{B}D \\
 &\quad + B\bar{C}\bar{D} + \bar{A}BC
 \end{aligned}$$

S<sub>0</sub> = ?

		CD	00	01	11	10
AB	00		1			1
	01	1			1	
	11		1			1
	10	1		1		

$$\begin{aligned}
 S_0 &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\
 &\quad + AB\bar{C}D + ABC\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD
 \end{aligned}$$

3)  $S_0$  with XOR!

$$S_0 = \bar{A}\bar{B}(\bar{C}D + C\bar{D}) + \bar{A}B(CD + \bar{C}\bar{D}) + A\bar{B}(\bar{C}D + C\bar{D}) + AB(\bar{C}\bar{D} + CD)$$

$$S_0 = \bar{A}\bar{B}(C \oplus D) + \bar{A}B(\bar{C} \oplus D) + A\bar{B}(C \oplus D) + AB(\bar{C} \oplus D)$$


$$S_0 = (C \oplus D)(\bar{A}\bar{B} + A\bar{B}) + (\bar{C} \oplus D)(\bar{A}B + AB)$$

$$= (C \oplus D)(\overline{A \oplus B}) + (\bar{C} \oplus D)(A \oplus B) \quad (1)$$

$$S_0 = (C \oplus D) \oplus (A \oplus B)$$

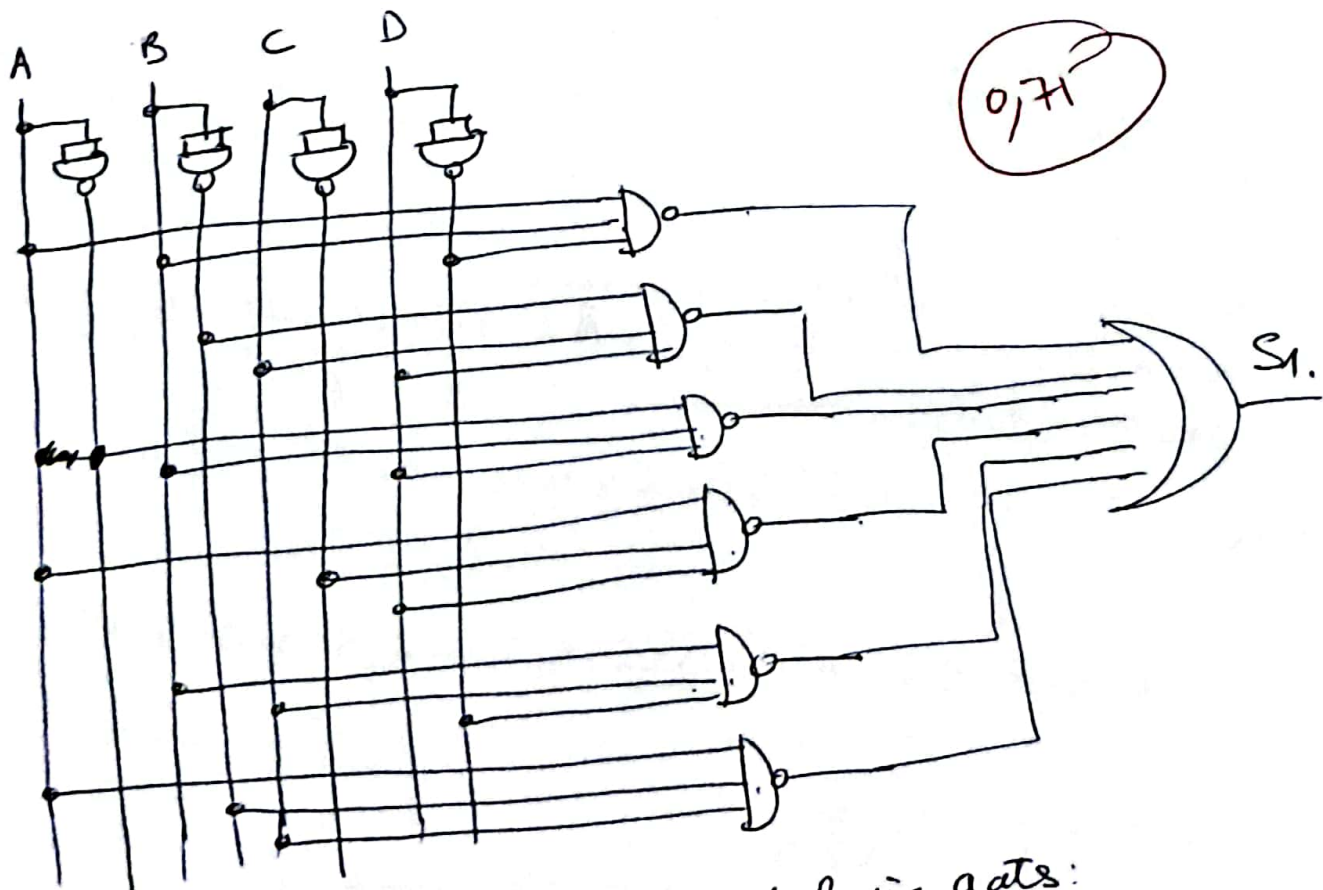4)  $S_1$  circuit with only NAND gates:

$$S_1 = \bar{S}_1 = \overline{AB\bar{D}} \cdot \overline{BCD} \cdot \overline{ABD} \cdot \overline{ACD} \cdot \overline{BC\bar{D}} \cdot \overline{A\bar{B}C}$$




5)  $S_1$  circuit with DEC 3x8 and logic gates:

$$S_1 = A[B\bar{C}\bar{D} + B\bar{C}D + B\bar{C}\bar{D} + \bar{B}\bar{C}D + \bar{B}\bar{C}\bar{D} + \bar{B}C\bar{D}] + B\bar{C}\bar{D} + \bar{B}C\bar{D} + \bar{A}[B\bar{C}D + B\bar{C}\bar{D}]$$

(9) 
$$= A[B\bar{C}\bar{D} + \bar{B}\bar{C}D + \bar{B}C\bar{D}] + B\bar{C}\bar{D} + \bar{B}C\bar{D} + \bar{A}BCD + B\bar{C}\bar{D}$$

100 S <sub>4</sub>	001 S <sub>1</sub>	010 S <sub>2</sub>	110 S <sub>6</sub>	011 S <sub>3</sub>	111 S <sub>7</sub>	101 S <sub>5</sub>
-----------------------	-----------------------	-----------------------	-----------------------	-----------------------	-----------------------	-----------------------


-5-

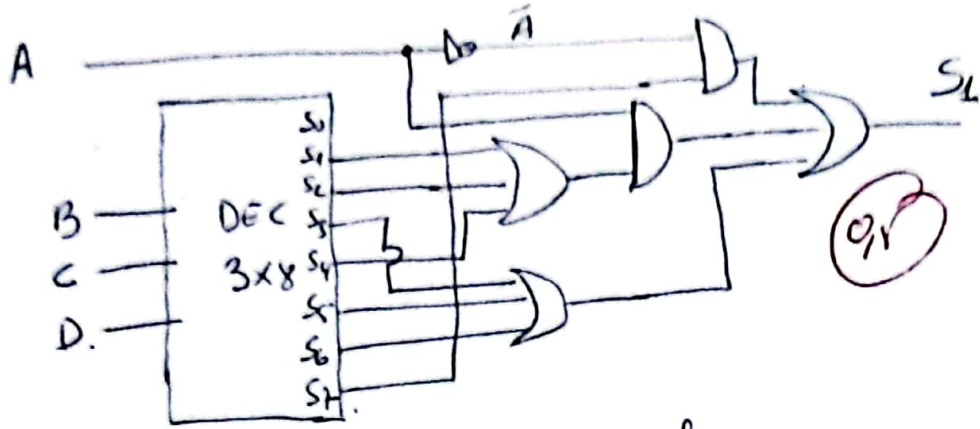

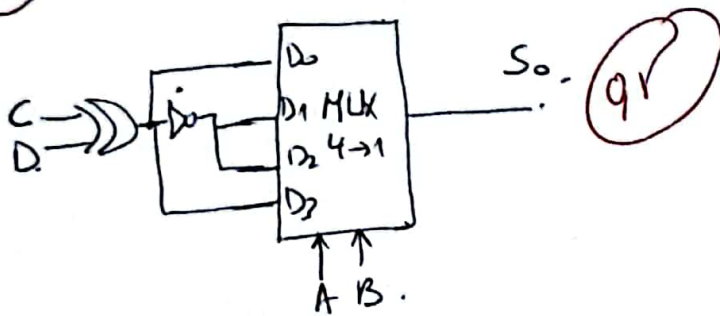6)  $S_0$  with a MUX 4x1 and logic gates:

$$S_0 = \bar{A}\bar{B}(C \oplus D) + \bar{A}B(\overline{C \oplus D}) + A\bar{B}(C \oplus D) + AB(\overline{C \oplus D})$$


$\begin{matrix} 00 & 01 & 10 & 11 \\ D_0 & D_1 & D_2 & D_3 \end{matrix}$



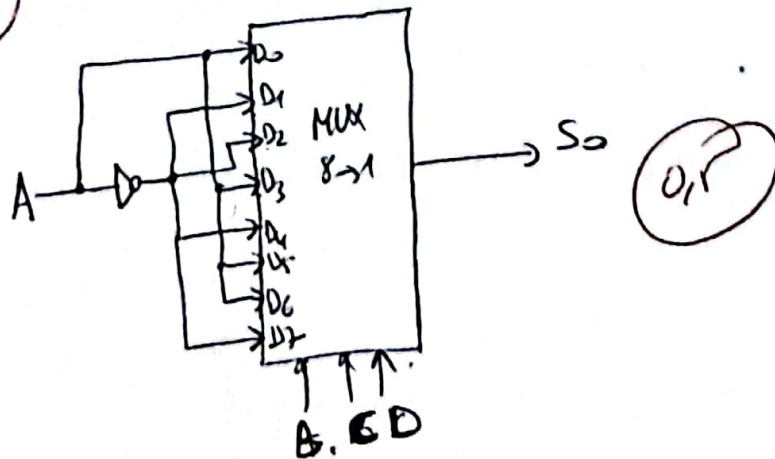7)  $S_0$  with a MUX 8x1 and inverters

$$S_0 = \bar{A}[\bar{B}\bar{C}D + \bar{B}C\bar{D} + B\bar{C}\bar{D} + BCD] + A[\bar{B}\bar{C}D + \bar{B}C\bar{D} + B\bar{C}\bar{D} + BCD]$$

$\begin{matrix} 001 & 010 & 100 & 111 \\ D_0 & D_1 & D_2 & D_3 \end{matrix}$



Remark:

the same result can be obtained directly from the analysis of the truth table.